

Nilsson/Riedel

Homework on Superposition

- 2.26. Use the principle of superposition to find the voltage v_o in the circuit in Fig. P2.26.

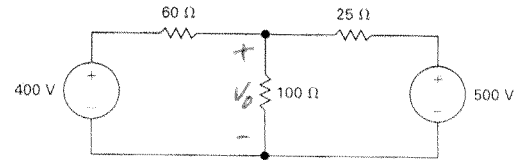


Figure P2.26

- 2.27. Use the principle of superposition to find the current i_o in the circuit in Fig. P2.27.

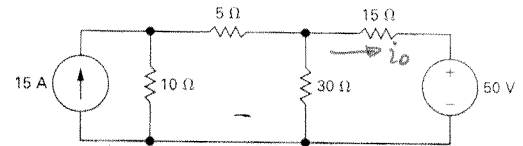


Figure P2.27

- 2.28. Use the principle of superposition to find v_o in the circuit in Fig. P2.28.

