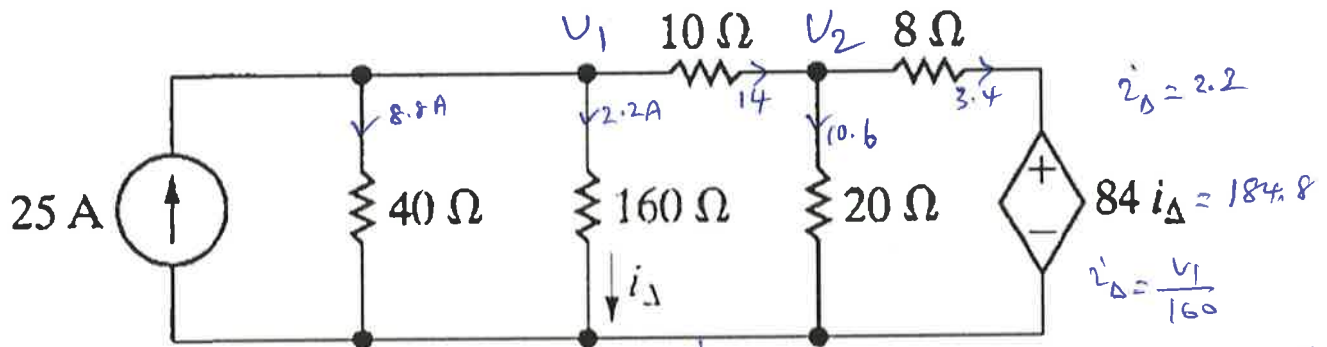


1 a) Use the node-voltage method to find the total power developed in the circuit.

$V_1 = 352 \text{ Volt}$
 $V_2 = 212 \text{ volt}$

b) Check your answer by finding the total power absorbed in the circuit.



$$\frac{V_1 - V_2}{10} + \frac{V_1}{160} + \frac{V_1}{40} - 25 = 0$$

$$16(V_1 - V_2) + V_1 + 4V_1 - 4000 = 0$$

$$21V_1 - 16V_2 = 4000 \quad \text{--- (1)}$$

$$-53V_1 + 88V_2 = 0 \quad \text{--- (2)}$$

$$V_1 = \frac{88V_2}{53}$$

$$21 \times \frac{88}{53} V_2 - 16V_2 = 4000$$

$$21 \times 88 V_2 - 53 \times 16 V_2 = 53 \times 4000$$

$$V_2 = \frac{53 \times 4000}{(21 \times 88 - 53 \times 16)} = \frac{212,000}{1848 - 848} = 212 \text{ volt}$$

$$V_1 = \frac{88}{53} \times V_2 = 352 \text{ volt}$$

$V_1 = 352 \text{ Volt}$
 $V_2 = 212 \text{ Volt}$

(a) $P_{25A} = V_1 \times 25 = 352 \times 25$
 $P_{dev} = 8,800 \text{ W}$

absorb $P_{84i_D} = 184.8 \times \frac{(212 - 184.8)}{8} = 628.32 \text{ W}$

$P_{dev} = 9,428 \text{ W}$


$$P_{abs} = 8.8^2 \times 40 + 2.2^2 \times 160 + 14^2 \times 10 + 10.6^2 \times 20 + 3.4^2 \times 8$$

$$= 3097.6 + 774.4 + 1960 + 2247.2 + 92.48$$

$P_{abs} = 8172 \text{ W}$

$P_{abs} = 8172 + 628 = 8800 \text{ W}$

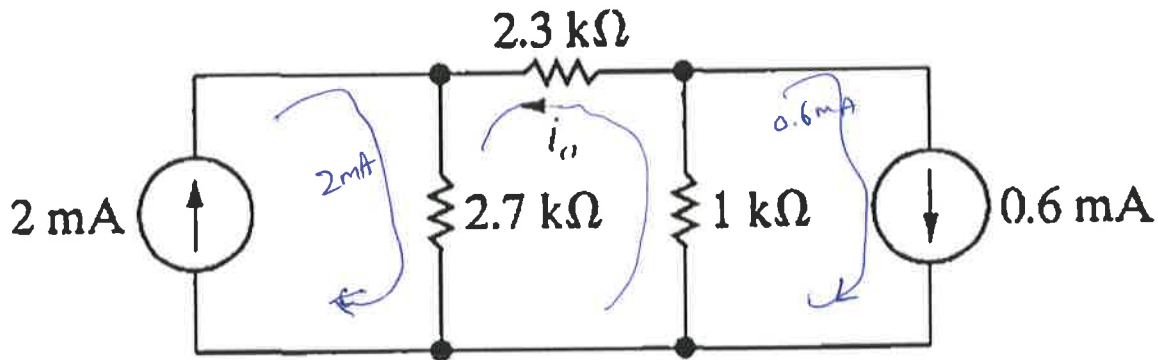
2. Use a series of source transformations to find the current i_o in the circuit. $i_o = -1 \text{ mA}$



$$-(i_o + 0.6) - 2.3 i_o - 2.7(i_o + 2) = 0$$

$$-6i_o = 6$$


$$i_o = -1 \text{ mA}$$

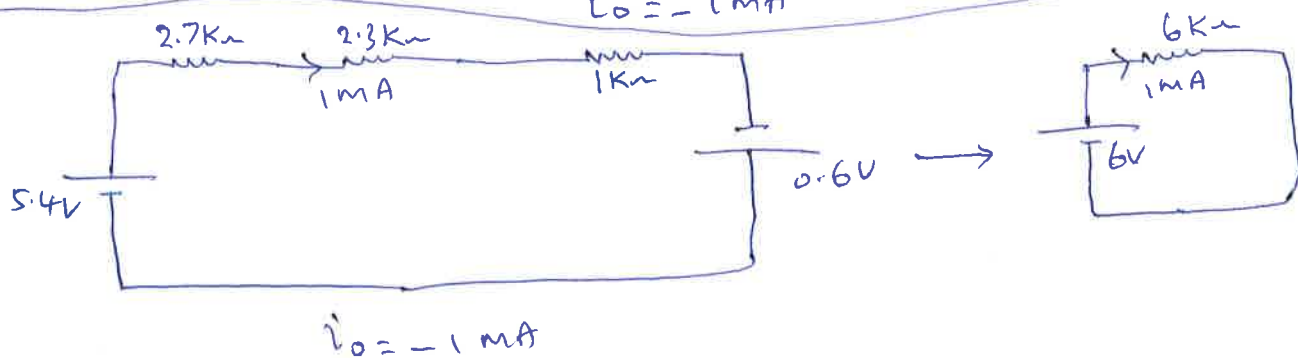

3. Repeat the above problem using the mesh-current method.

4. Use your method of choice to find the current i_o .

2 mA

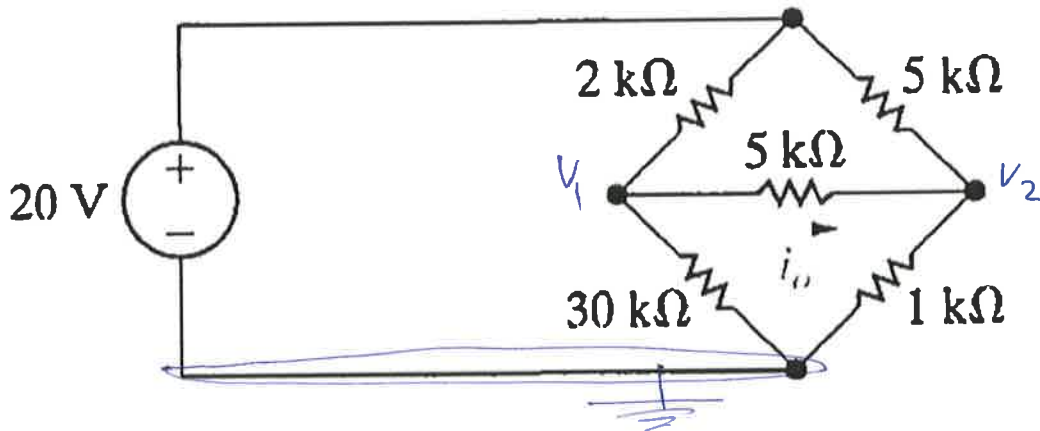

$$\frac{V_1}{30} + \frac{V_1 - V_2}{5} + \frac{V_1 - 20}{2} = 0$$

$$V_1 + 6(V_1 - V_2) + 15(V_1 - 20) = 0$$

$$22V_1 - 6V_2 - 300 = 0$$

$$22(7V_2 - 20) - 6V_2 - 300 = 0$$

$$154V_2 - 6V_2 - 440 - 300 = 0$$

$$V_2 = 5 \text{ volt}, \quad V_1 = 35 - 20 = 15 \text{ volt}$$

$$i_o = \frac{15 - 5}{5} = 2 \text{ mA}$$

$$i_o = 2 \text{ mA}$$

$$\frac{V_2}{1} + \frac{V_2 - V_1}{5} + \frac{V_2 - 20}{5} = 0$$


$$5V_2 + V_2 - V_1 + V_2 - 20 = 0$$

$$-V_1 + 7V_2 - 20 = 0$$

$$V_1 = 7V_2 - 20 \quad \text{--- (2)}$$

5. Use your method of choice to find the voltage v_o .

3.2V

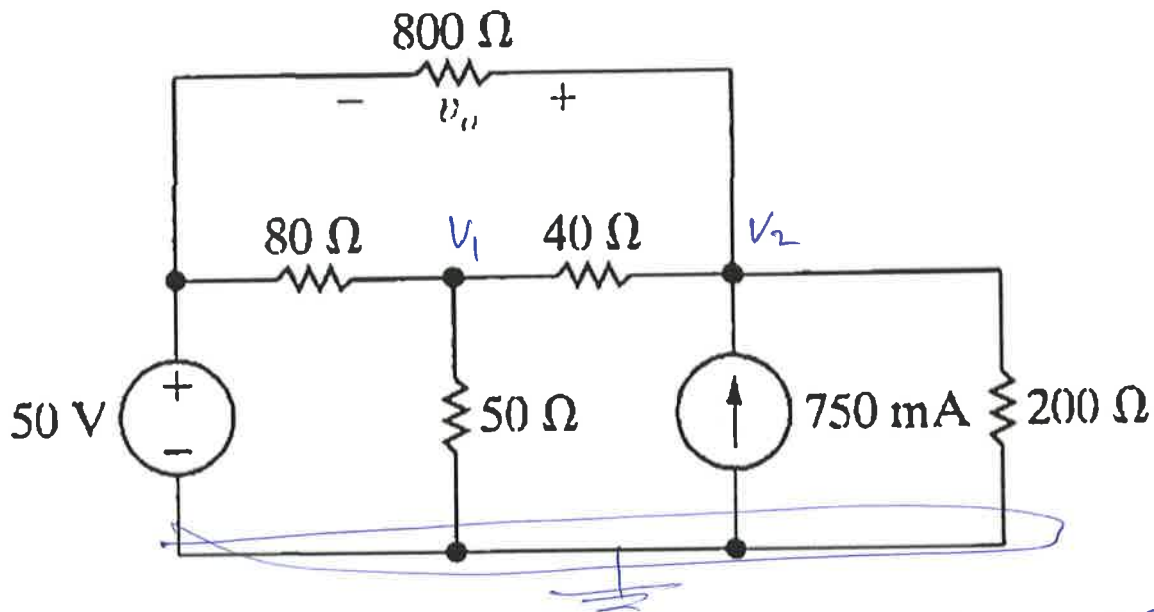

$$\frac{V_1 - 50}{80} + \frac{V_1}{50} + \frac{V_1 - V_2}{40} = 0$$

$$5V_1 - 250 + 8V_1 + 10V_1 - 10V_2 = 0$$

$$23V_1 - 10V_2 - 250 = 0$$

$$23V_1 - 10(0.8V_1 + 26) - 250 = 0$$

$$23V_1 - 8V_1 - 260 - 250 = 0$$

$$15V_1 = 510$$

$$V_1 = 34 \text{ volt}$$

$$V_2 = 53.2 \text{ volt}$$

$$V_o = V_2 - 50 = 53.2 - 50 = 3.2 \text{ volt}$$

$$V_o = 3.2 \text{ volt}$$

$$\frac{V_2}{200} - 0.75 + \frac{V_2 - V_1}{40} + \frac{V_2 - 50}{800} = 0$$

$$4V_2 - 600 + 20V_2 - 20V_1 + V_2 - 50 = 0$$

$$-20V_1 + 25V_2 - 650 = 0$$

$$25V_2 = 20V_1 + 650$$

$$V_2 = 0.8V_1 + 26$$